

REPORT-2

Jaiveer Kiran S. K ee22b042

MAY 2025


Contents:



1. *MOS characterization*
2. *Opamp Design*
3. *Diode and Resistors*
4. *Bandgap reference voltage generator*

MOS Characterization :



- G_m/I_d parameter is used as a key design parameter because it is independent of the size of the MOSFET and the range of values is limited to **1-30**.
- More suited for small channel mosfets as well.



TSMC 180nm Nmos:

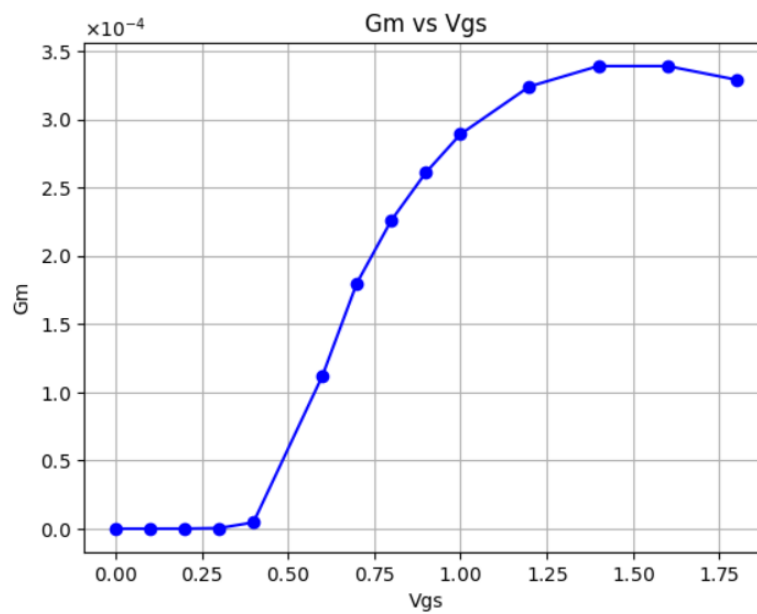

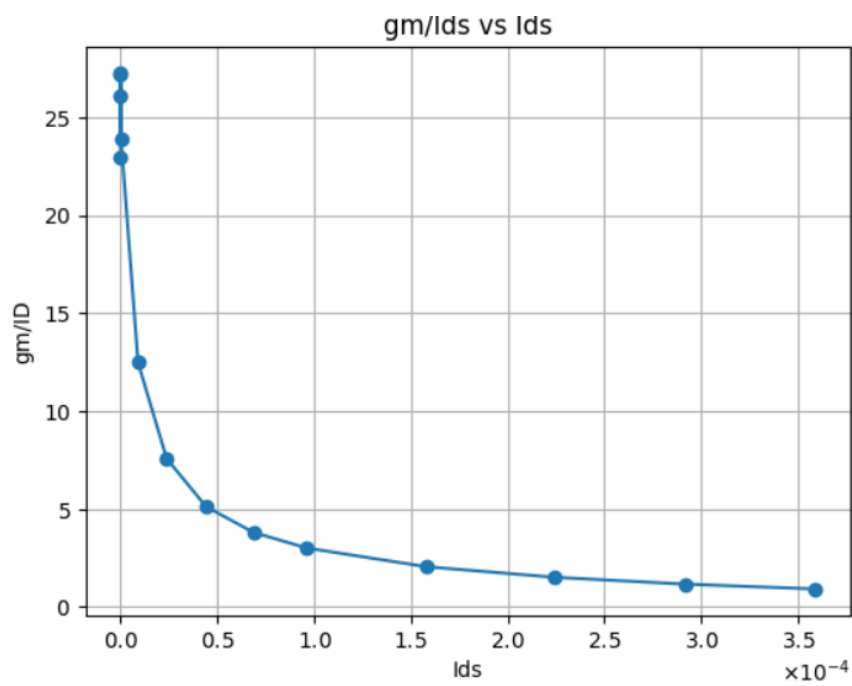 

TSMC 180nm Pmos:

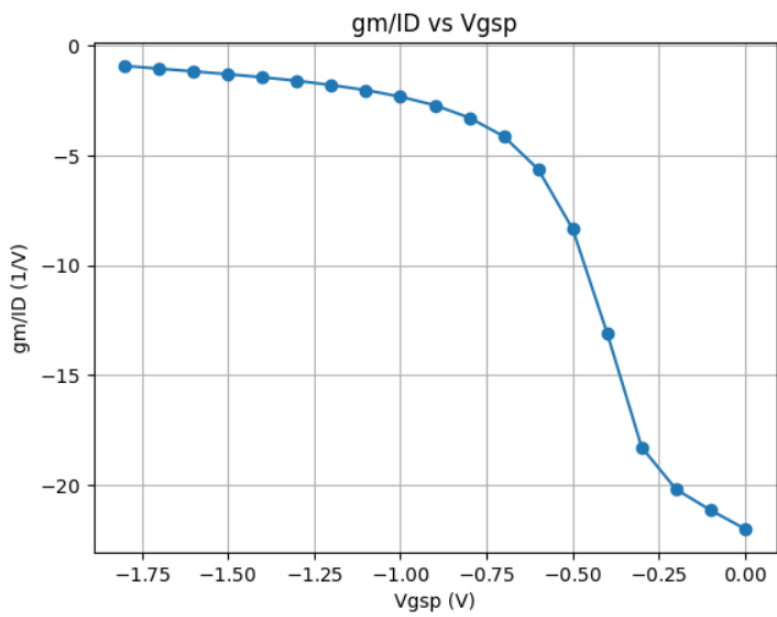 

  

Opamp Design:

Bias current:

$$f_{\text{UGB}} = \frac{g_{m_1}}{2\pi C_c} = \frac{\left(\frac{g_{m_1}}{I_D}\right) \cdot I_D}{2\pi C_c}$$

- Assume the Bandwidth needed for the Opamp used in bandgap reference circuit is **40 MHz**.
- To have a higher gain the mosfets are to be biased to operate in moderate inversion ie. **Gm/Id between 15 to 20** for the input Nmos.
- Let the miller capacitor be 1pF.

$$\begin{aligned} I_d &\approx \frac{40 \times 10^6 \times 2\pi \times 10^{-12}}{15} \\ &\approx 16.75\mu A \\ I_{\text{tail}} &= 2 \times I_d \\ &\approx 33.5\mu A \end{aligned}$$

- Acceptable Gm/Id range for **Tail Mosfet: 17–23**. This corresponds to weak-to-moderate inversion, providing higher output resistance (more accurate differential stage) and lower power consumption.
- From the plots above the preferred Ids per unit width :

$$\approx 1.5625\mu A$$

- No. of fingers:

$$m \approx \frac{33.5\mu}{1.5625\mu} = 22$$

1. Observed Tail Current $28.9\mu A$.

2. Observed Gm/Id = 22.076 .

3. No.of fingers used 30.

- For nmos active load at bias stage Gm/Id preferred : 17-20.
- Current per unit width is the same as that of the tail: $1.5625\mu A$. Thus for $m = 3$, $I_{\text{bias}} \approx 3 \times 1.5625\mu A \approx 4.6875\mu A$.
- The bias current used is **5 μA** .

Mosfet Sizing:

1. 2nd Stage (Method -1):

- The DC gain obtained from 1st stage designed is $\approx 56dB$. Gain needed from the 2nd stage $\approx 30dB$.

$$A_v = 30 \text{ dB}$$

$$\frac{g_{m10}}{g_{ds10} + g_{ds11}} \approx 3.32$$

$$\left(\frac{g_{m10}}{I_D} \right) I_D \approx 3.32 \times (g_{ds10} + g_{ds11})$$

$$I_D \approx \frac{3.32 \times 10^{-4}}{15}$$

$$\approx 23 \mu A$$

$$\text{current per finger} = 1.5625 \mu A$$

$$\text{No. of fingers for 2nd stage active load} \approx \frac{23}{1.5625}$$

$$\approx 15$$

 


Figure 1: DC gain achieved but PM is only 30 degrees

- This is because of lower value of G_{m10} , the Zero is at lower frequency. To push the zero away a zero-canceling resistor of value 2K is added.

 


Figure 2: PM after adding Zero cancelling resistor = 70 degrees.

- **disadvantages:** Presence of a resistor, lower current at 2nd stage (Very poor Slew Rate).

2. 2nd Stage (Method -2):

- Instead of adding a zero-cancelling resistor, we can increase the current in the 2nd stage, maintaining the G_m/I_d ratio the same (DC gain depends on G_m/I_d), to increase G_m and push Zero away until PM is 70 degrees.
- Observed Current is $286 \mu A$ current.

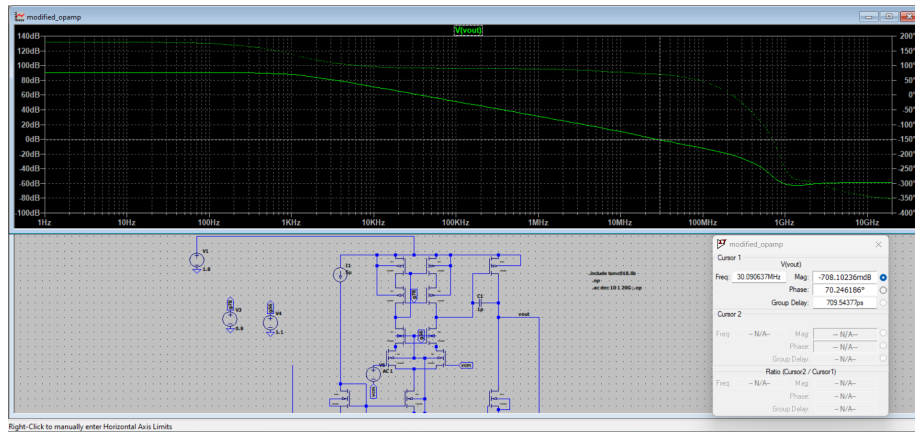


Figure 3: 2-nd stage biased from Method -2

Diode and Resistors:

- We can assume V_{ref} to be 1.11v and plot diode characteristics at an average temperature of 40 degrees.

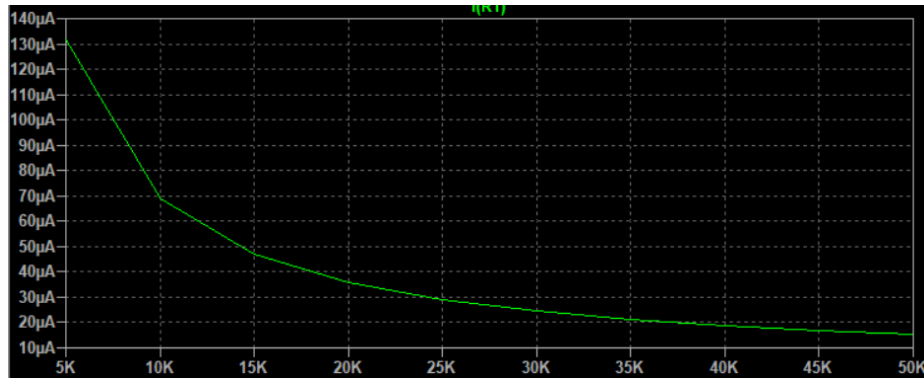


Figure 4: Current in 1N4148 vs R_2

 


Figure 5: V_{ref} obtained vs R_2 at 40°C

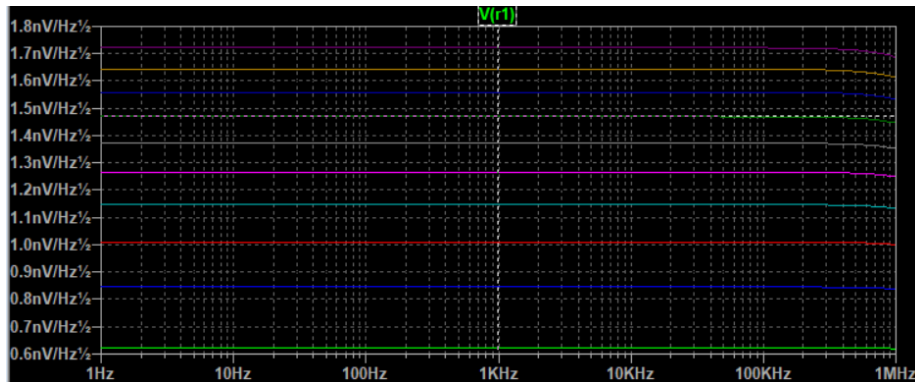


Figure 6: noise PSD vs R2

- There is a trade-off between Power consumed, noise and Vref obtained.
- So to balance the effects, **R2 is taken around 20k** which corresponds to current of about $40\mu A$.

Current Mirrors:

- Operate in weak to moderate inversion, leading to higher output resistance and better current matching. Required G_m/I_D : 17-22.
- From the g_m/I_D vs I_{DS} plot of PMOS, the current per unit width is approximately $1.25 \mu A$.
- No. of fingers:

$$m \approx \frac{40\mu}{1.25\mu} = 32$$

Bandgap reference voltage generator:

- Temperature Coefficient of resistors used: 0.0001 ppm/C (only linear term considered).

 
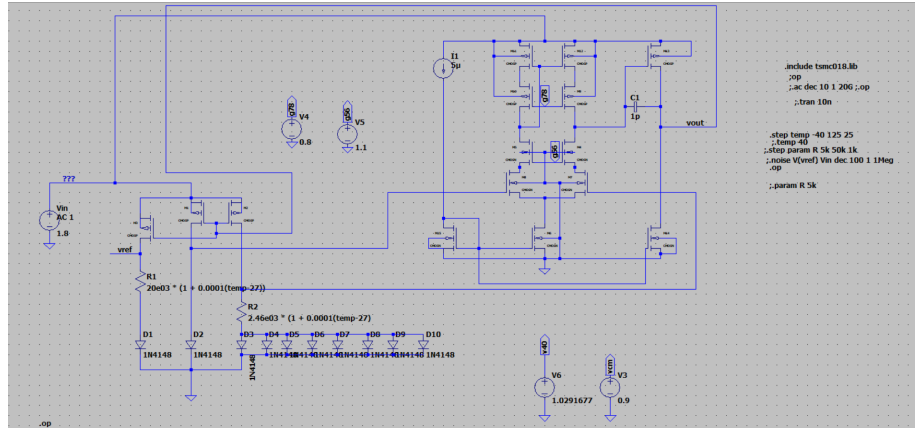


Figure 7: Reference voltage generated

 


Figure 8: Error in Vref wrt values at 40°C

Calculations:

$$|\text{slope of PTAT}| = |\text{slope of CTAT}|$$

$$\frac{k \ln(N)}{q} \cdot \frac{R_2}{R_1} = 2 \times 10^{-3}$$

$$\frac{R_2}{R_1} = \frac{2 \times 10^{-3}}{\frac{k \ln(8)}{q}} = \frac{2 \times 10^{-3}}{86 \times 10^{-6} \cdot \ln(8)}$$

$$\approx 11.184$$

Observations:

- From earlier analysis, $R_2=20\text{ K}$.
- To balance the slopes $R_1=2.46\text{ K}$.
- CTAT slope observed: -2.34mV/C .
- $V_{\text{ref}} = 1.0289\text{ V}$. Range of errors: $(-30\text{mV to } 3\text{mV})$.