

report5

Jaiveer Kiran S. K ee22b042

July 2025

Target Specifications:

- Output Voltage = $0.5V \pm 1\%$
- Supply Voltage = $1.8V \pm 10\%$
- Power Consumption $< 1mW$
- Temperature Range: $-40^{\circ}C$ to $125^{\circ}C$

Characteristics:

Mosfets:

- Model: TSMC 65nm GP nch,pch.

 


Figure 1: NMOS characteristics

 


Figure 2: PMOS characteristics

Diodes:

- Model: TSMC 65nm **ndio_25**
- Non-ideality factor (η): 0.84.
- CTAT slope: -1.72mv/C .

 


Figure 3: Diode characteristics

Bias Currents:

$$(I_{\text{total}})_{\text{max}} = \frac{1000 \mu\text{W}}{1.8 \text{ V}} = 566.6 \mu\text{A}$$

Current Division

- Opamp used in regulated cascode: $25 \mu\text{A} + 5 \mu\text{A} = 30 \mu\text{A}$
- Regular Opamp: $45 \mu\text{A} + 5 \mu\text{A} = 50 \mu\text{A}$
- Bias stage: $5 \mu\text{A}$
- Branch current in core bandgap: $100 \mu\text{A} + 100 \mu\text{A} + 100 \mu\text{A} = 300 \mu\text{A}$

Design Equations

•

$$\begin{aligned} \frac{\frac{k}{q} \ln(n) \eta}{R_1} &= \frac{0.00174}{R_2} \\ \Rightarrow \frac{R_2}{R_1} &\approx 11.58 \end{aligned} \tag{1}$$

•

$$100 \mu = \frac{\frac{k}{q} (300) \ln(n) \eta}{R_1} + \frac{0.709}{R_2} \tag{2}$$

Solving:

$$R_1 = 1063.76 \Omega, \quad R_2 \approx 12,310 \Omega$$

$$\begin{aligned} R_3 &= \frac{0.5}{100 \mu\text{A}} \\ &= 5k \Omega \end{aligned}$$

Bandgap Reference:

 


Figure 4: Output voltage

 


Figure 5: ZTAT current

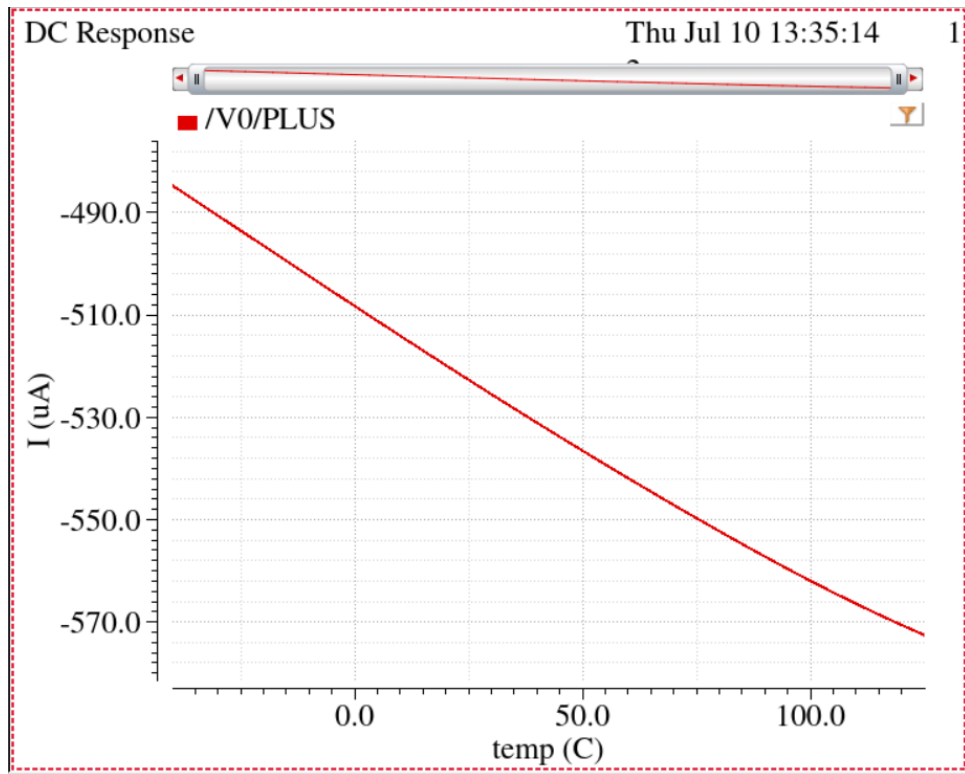


Figure 6: total current

 


Figure 7: CTAT and PTAT current

 


Figure 8: bandgap circuit

Observations:

- Reference voltage at 27C: 0.510mV.
- Maximum current used: 572.5 uA.